

Enigmas, etc.

DC Load Pull

■ Takashi Ohira ^{ID}

Continued from last month, a single series diode rectifier is excited by a sinusoidal voltage source through a series inductor. To adjust the diode's on-duty cycle, we now employ a variable resistor for the dc load, as shown in Figure 1. Can we predict the specific resistance R_o that leads the diode to a 50% on-duty cycle? Choose the correct answer from the following four candidates for R_o :

- a) $2fL$
- b) $2\pi fL$
- c) $2\pi^2 fL$
- d) $2\pi^3 fL$.

Takashi Ohira (ohira@tut.jp) is with Toyohashi University of Technology, Aichi 441-8580, Japan. He is a Life Fellow of IEEE.

Digital Object Identifier 10.1109/MMM.2023.3265538
Date of current version: 3 June 2023

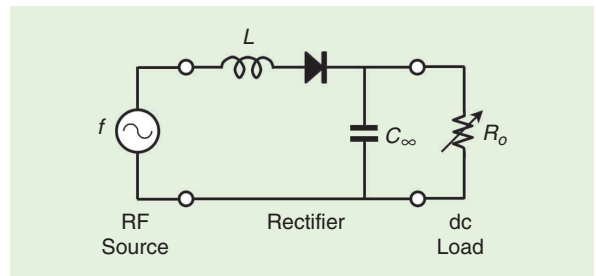


Figure 1. Single series diode rectifier from last month, now terminated by a variable resistor for the dc load-pull thought experiment.



Errata

In a recent "Health Matters" column [1], on page 19 of the magazine, there was an error in the following sentence: "For base station antennas transmitting at 1,990 MHz, the FCC limit for the public is 1.27 mW/cm² (12.7 W/m²)."

Digital Object Identifier 10.1109/MMM.2023.3276096
Date of current version: 3 June 2023

A digit was missing, and the key phrase "for frequencies above 1,500 MHz" was left out. The sentence should read, "For base station antennas transmitting at 1,990 MHz, instead of a value of 1.327 mW/cm² (13.27 W/m²), the FCC limit for the public is capped by 1 mW/cm² (10 W/m²) for operating frequencies above 1,500 MHz."

In addition, power densities listed in Table 1 should be in W/m² and not W/cm².

The *IEEE Microwave Magazine* regrets the errors.

Reference

- [1] J. C. Lin, "RF health safety limits and recommendations [Health Matters]," *IEEE Microw. Mag.*, vol. 24, no. 6, pp. 18–77, Jun. 2023, doi: 10.1109/MMM.2023.3255659.

