

Enigmas, etc.

Rectifier Efficiency

Takashi Ohira

half-wave rectifier consists of a choking inductor *L*, an ideal diode, and a smoothing capacitor *C*, as shown in Figure 1. We assume for simplicity that *L* has infinite inductance, *C* has infinite capacitance, and there is no power dissipation in the diode. The rectifier is excited by a 50- Ω sinusoidal-wave source and produces dc power to a 50- Ω load. What is the RF-to-dc power conversion efficiency?



Figure 1. A single-series diode rectifier working in a 50- Ω system.

Solution to the September/October "Enigmas, etc." The correct answer to the problem presented in the September/October 2017 installment of "Enigmas, etc." is b).

From the definitions of k and Q, it is straightforward to deduce

$$kQ = \frac{M}{L}\frac{\omega L}{R} = \frac{\omega M}{R} = \tan 2\theta.$$

This relation is projected on a persuasive chart in Figure 2. Answers to the July/August and September/October

Takashi Ohira (ohira@tut.jp) is with Toyohashi University of Technology, Aichi, Japan. Ohira is a Fellow of the IEEE.

> Digital Object Identifier 10.1109/MMM.2017.2739558 Date of publication: 12 December 2017

quizzes are summarized in a system of easy-to-remember equations,

$$\begin{cases} kQ = \tan 2\theta \\ \eta_{\max} = \tan^2 \theta \end{cases}$$

by way of θ . For example, at least $kQ = 4\sqrt{5}$ is needed to achieve 80 % in efficiency.



Figure 2. A subtriangle created to visually demonstrate what kQ is.

Reviewing this relation, one may notice that k and Q work together as a single quantity. That is exactly right. Actually, in many cases, they cannot be evaluated separately. Even in such situations, kQ still works as a figure of merit [1]. The kQ theory, first introduced in magnetic couplers, has been found applicable to any scheme of a reciprocal two-port network for diverse power-transfer systems.

Reference

[1] T. Ohira, "The kQ product as viewed by an analog circuit engineer," *IEEE Circuits Syst. Mag.*, vol. 17, no. 1, pp. 27–32, Feb. 2017.