

Enigmas, etc.

Solution to Last Month's Quiz

■ Takashi Ohira

It takes tough work, in general, to analytically characterize the power conversion efficiency of non-linear circuits. However, for this puzzle, we can exploit the two equations

$$\begin{bmatrix} V_O & I_O \\ V_P & I_P \\ V_Q & I_Q \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 50 & 1 \end{bmatrix} I_1 \quad (1)$$

$$I_1 = \pi I_2 \quad (2)$$

both already derived in this “Enigma” series. Remember that subscript *O* stands for dc, *P* for in phase, and *Q* for the quadrature Fourier components of the input waveform. Also remember that I_1 and I_2 denote RF source current and dc load current, respectively (see Figure 1).

First, from (1), the RF input power is calculated as

$$\begin{aligned} P_{in} &= \frac{1}{2} [V_P \ V_Q] \begin{bmatrix} I_P \\ I_Q \end{bmatrix} \\ &= \frac{1}{8} [0 \ 50] \begin{bmatrix} 0 \\ 1 \end{bmatrix} I_1^2 \\ &= \frac{25}{4} I_1^2. \end{aligned} \quad (3)$$

Then, from (2), the dc output power is calculated as

$$\begin{aligned} P_{out} &= 50 I_2^2 \\ &= \frac{50}{\pi^2} I_1^2. \end{aligned} \quad (4)$$

Takashi Ohira (ohira@tut.jp) is with the Toyohashi University of Technology, Aichi, 441-8580, Japan. He is a Life Fellow of IEEE.

Digital Object Identifier 10.1109/MMM.2022.3203946
Date of current version: 2 November 2022

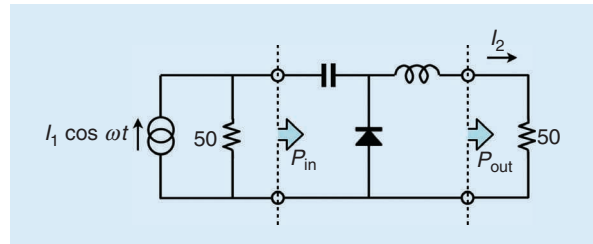


Figure 1. The circuit diagram for analysis.

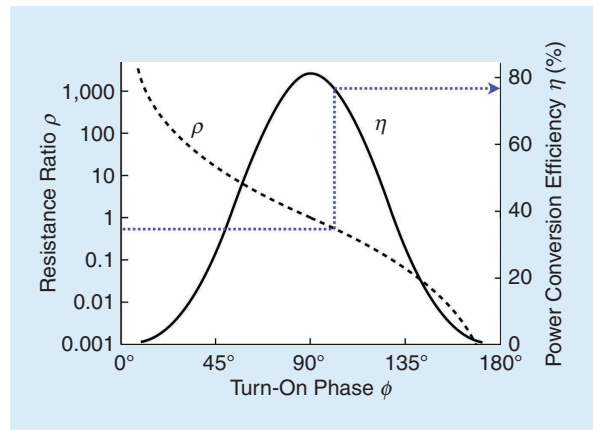


Figure 2. The arrowed crank guides us to the power conversion efficiency.

Finally, from the quotient of (4) to (3), we find the power conversion efficiency as

$$\begin{aligned} \eta &= \frac{P_{out}}{P_{in}} \\ &= \frac{8}{\pi^2} \\ &\approx 0.81. \end{aligned} \quad (5)$$

Therefore, the correct answer to last month's quiz is "c."

In this puzzle, the source and load resistors are both set to 50Ω for simplicity. However, they are not always so in practical systems. To find the general solution valid for arbitrary resistances, we need more work [1]. The calculus process is too complicated to describe in this brief column. However, the final formula is amazingly elegant:

$$\eta = \frac{8}{\pi^2} \sin^3 \phi. \quad (6)$$

Note that ϕ denotes the turn-on phase stemming from

$$\tan \phi - \phi = \frac{\pi}{\rho - 1} \quad (7)$$

where ρ stands for the source-to-load resistance ratio R_1/R_2 .

Although (6) lets us explicitly find η from ϕ , the transcendent equation (7) cannot be solved algebraically for ϕ . We therefore take a graphical approach instead. In Figure 2, (6) and (7) are projected onto a plane with common abscissa. This chart enables us to quickly find η from a given ρ by way of ϕ . For example,

we start from $\rho = 0.58$ on the left-side ordinate. Going along the cranked line, the dashed curve finds $\phi = 100^\circ$, and, finally, the solid curve finds $\eta = 77\%$. This chart also confirms (5), especially signifying that η reaches its peak, i.e., 81% when $R_1 = R_2$. The remaining 19% of the total input energy dissipates into second and higher order harmonics due to the diode's nonlinearity.

Since the efficiency is limited to 81% for this basic rectifier, one may expect even higher efficiency in future advanced RF system applications. To address this expectation, we have a viable solution exploiting a harmonic reaction technique called the *class E diode rectifier* [2], [3].

References

- [1] T. Ohira, "Power efficiency and optimum load formulas on RF rectifiers featuring flow-angle equations," *IEICE Electron. Exp.*, vol. 10, no. 11, pp. 1–9, Jun. 2013, doi: 10.1587/elex.10.20130230.
- [2] W. A. Nitz et al., "A new family of resonant rectifier circuits for high frequency DC-DC converter applications," in *Proc. 3rd Annu. IEEE Appl. Power Electron. Conf. Expo.*, New Orleans, LA, USA, Feb. 1988, pp.12–22, doi: 10.1109/APEC.1988.10546.
- [3] T. Ohira, "Linear algebra elucidates class-E diode rectifiers," *IEEE Microw. Mag.*, vol. 23, no. 12, Dec. 2022.



Are You Moving?

Don't miss an issue of this magazine—
update your contact information now!

Update your information by:

E-MAIL: address-change@ieee.org

PHONE: +1 800 678 4333 in the United States
or +1 732 981 0060 outside
the United States

If you require additional assistance
regarding your IEEE mailings,
visit the IEEE Support Center
at supportcenter.ieee.org.

IEEE publication labels are printed six to eight weeks
in advance of the shipment date, so please allow sufficient
time for your publications to arrive at your new address.



© ISTOCKPHOTO.COM/BRIANAJACKSON